### zk-SNARK

Distributed Lab

Sep 5, 2024



1/28

Distributed Lab zk-SNARK I 1/28 Sep 5, 2024

## Plan

- What is zk-SNARK?
- 2 Arithmetic Circuits
- Arithmetic Circuits
- 4 Rank-1 Constraint System
- 5 Quadratic Arithmetic Program



2/28

Distributed Lab zk-SNARK I 2 / 28 Sep 5, 2024

Distributed Lab zk-SNARK I 3 / 28 Sep 5, 2024

### **Definition**

**zk-SNARK** – Zero-Knowledge Succinct Non-interactive ARgument of Knowledge.

#### **Definition**

**zk-SNARK** – Zero-Knowledge Succinct Non-interactive ARgument of Knowledge.

• Argument of Knowledge — a proof that the prover knows the data (witness) that resolves a certain problem, and this knowledge can be "extracted".

#### **Definition**

**zk-SNARK** – Zero-Knowledge Succinct Non-interactive ARgument of Knowledge.

- Argument of Knowledge a proof that the prover knows the data (witness) that resolves a certain problem, and this knowledge can be "extracted".
- Succinctness the proof size and verification time is relatively small relative to the computation size and typically does not depend on the size of the data or statement.

4 / 28

#### **Definition**

**zk-SNARK** – Zero-Knowledge Succinct Non-interactive ARgument of Knowledge.

- Argument of Knowledge a proof that the prover knows the data (witness) that resolves a certain problem, and this knowledge can be "extracted".
- Succinctness the proof size and verification time is relatively small relative to the computation size and typically does not depend on the size of the data or statement.
- **Non-interactiveness** to produce the proof, the prover does not need any interaction with the verifier.

4 / 28

#### **Definition**

**zk-SNARK** – Zero-Knowledge Succinct Non-interactive ARgument of Knowledge.

- Argument of Knowledge a proof that the prover knows the data (witness) that resolves a certain problem, and this knowledge can be "extracted".
- Succinctness the proof size and verification time is relatively small relative to the computation size and typically does not depend on the size of the data or statement.
- **Non-interactiveness** to produce the proof, the prover does not need any interaction with the verifier.
- **Zero-Knowledge** the verifier learns nothing about the data used to produce the proof, despite knowing that this data resolves the given problem and that the prover possesses it.

Distributed Lab zk-SNARK I 4 / 28 Sep 5, 2024 4 / 28

Well... Let's take a look at some example.

Distributed Lab zk-SNARK I 5 / 28 Sep 5, 2024 5 / 28

Well... Let's take a look at some example.



Imagine you're part of a treasure hunt...

Well... Let's take a look at some example.



Imagine you're part of a treasure hunt...

...and you've found a hidden treasure chest...



5/28

Well... Let's take a look at some example.



Imagine you're part of a treasure hunt...

...and you've found a hidden treasure chest...





...but how to prove that without revealing the chest location?

**The Problem**: you have found a hidden treasure chest, and you want to prove to the organizer that you know its location without actually revealing that.



**The Problem**: you have found a hidden treasure chest, and you want to prove to the organizer that you know its location without actually revealing that.



We can retrieve some information from that:

Question #81673

What is a secret data? Who is a prover and who is a verifier?

6/28

**The Problem**: you have found a hidden treasure chest, and you want to prove to the organizer that you know its location without actually revealing that.



We can retrieve some information from that:

### Question #81673

What is a secret data? Who is a prover and who is a verifier?

**The Secret Data**: the exact treasure location.

The Prover: you.

The Verifier: the treasure hunt organizer.



Distributed Lab zk-SNARK I 6 / 28 Sep 5, 2024 6 / 28

Here is how we can apply the zk-SNARK to our problem:

 Argument of Knowledge: You need to create a proof that demonstrates you know the chest is.

Distributed Lab zk-SNARK I 7 / 28 Sep 5, 2024 7 / 28

Here is how we can apply the zk-SNARK to our problem:

- Argument of Knowledge: You need to create a proof that demonstrates you know the chest is.
- Succinct: The proof you provide is very small and concise. It doesn't
  matter how large the treasure map is or how many steps it took you
  to find the chest.

Here is how we can apply the zk-SNARK to our problem:

- Argument of Knowledge: You need to create a proof that demonstrates you know the chest is.
- Succinct: The proof you provide is very small and concise. It doesn't
  matter how large the treasure map is or how many steps it took you
  to find the chest.
- Non-interactive: You don't need to have a back-and-forth conversation with the organizer to create this proof.

Here is how we can apply the zk-SNARK to our problem:

- Argument of Knowledge: You need to create a proof that demonstrates you know the chest is.
- Succinct: The proof you provide is very small and concise. It doesn't
  matter how large the treasure map is or how many steps it took you
  to find the chest.
- Non-interactive: You don't need to have a back-and-forth conversation with the organizer to create this proof.
- Zero-Knowledge: The proof doesn't reveal any information about the actual location of the treasure chest.

Here is how we can apply the zk-SNARK to our problem:

- Argument of Knowledge: You need to create a proof that demonstrates you know the chest is.
- Succinct: The proof you provide is very small and concise. It doesn't
  matter how large the treasure map is or how many steps it took you
  to find the chest.
- Non-interactive: You don't need to have a back-and-forth conversation with the organizer to create this proof.
- Zero-Knowledge: The proof doesn't reveal any information about the actual location of the treasure chest.




Well... The golden coin where the pirates' sign is engraved is our zk-SNARK proof!

But the problems that we usually want to solve are in a slightly different format.

Distributed Lab zk-SNARK I 8 / 28 Sep 5, 2024 8 / 28

But the problems that we usually want to solve are in a slightly different format.

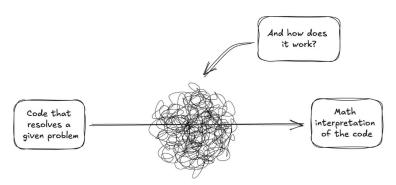When we need to prove that some element is in a merkle tree, we can't come to a verifier and give them a "coin"...



Distributed Lab zk-SNARK I 8 / 28 Sep 5, 2024 8 / 28

# **Arithmetic Circuits**

Distributed Lab zk-SNARK I 9 / 28 Sep 5, 2024

## The First Question To Resolve

The cryptographic tools we have learned in the previous lectures operate with numbers or certain primitives above them.

### Question?

How do we convert a program into a mathematical language?

Do not forget about succintness!

### **Boolean Circuits**

We can do that in a way like the computer does it - boolean circuits.


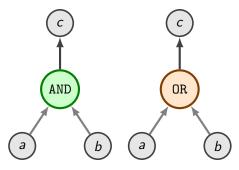


Figure: Boolean AND and OR Gates

Distributed Lab zk-SNARK I 11 / 28 Sep 5, 2024 11 / 28
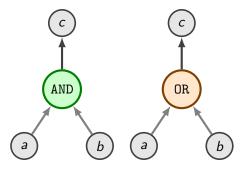
### **Boolean Circuits**

We can do that in a way like the computer does it - boolean circuits.



Α	В	A AND B	
0	0	0	
0	1	0	
1	0	0	
1	1	1	

Figure: AND Gate Truth Table

Figure: Boolean AND and OR Gates

#### Note

With any of  $\{AND, NOT\}$  or  $\{OR, NOT\}$  gates sets one can build any possible logical circuit, they are called **functionally complete** sets.

Distributed Lab zk-SNARK I 11 / 28 Sep 5, 2024 11 / 28

# Boolean Circuit Example

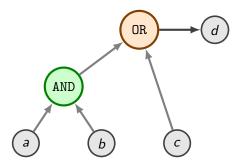


Figure: Example of a circuit evaluating d = (a AND b) OR c.

Distributed Lab zk-SNARK I 12 / 28 Sep 5, 2024 12 / 28

# Boolean Circuit Example

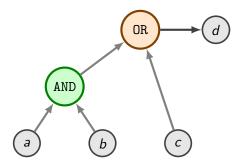


Figure: Example of a circuit evaluating d = (a AND b) OR c.

Boolean circuits receive an input vector of 0, 1 and resolve to true (1) or false (0); basically, they determine if the input values satisfy the statement.

The above circuit can be satisfied with the next values:

$$a = 1, \quad b = 1, \quad c = 0$$



Distributed Lab zk-SNARK I 12 / 28 Sep 5, 2024 12 / 28

### SHA-256 Boolean circuit

File	No. ANDs	No. XORs	No. INVs
sha256Final.txt	22,272	91,780	2,194

Figure: Stats of a SHA256 boolean circuit implementation.

More than 100000 gates. Impressive, doesn't it?

But it also shows how inconvenient the boolean circuits are.

## **Arithmetic Circuits**

### Arithmetic Circuits

Similar to Boolean Circuits, the **Arithmetic circuits** consist of gates and wires.

- ullet Wires: elements of some finite field  $\mathbb{F}$ .
- ullet Gates: addition  $(\oplus)$  and multiplication  $(\odot)$  corresponding to the field.

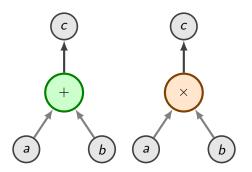


Figure: Addition and Multiplication Gates

```
Example
```

```
def multiply(a: F, b: F) -> F:
    return a * b
```

## Example

```
def multiply(a: F, b: F) -> F:
    return a * b
```

This can be represented as a circuit with only one (multiplication) gate:

$$r = a \times b$$

Distributed Lab zk-SNARK I 16 / 28 Sep 5, 2024 16 / 28

## Example

```
def multiply(a: F, b: F) -> F:
    return a * b
```

This can be represented as a circuit with only one (multiplication) gate:

$$r = a \times b$$

The witness vector (essentially, our solution vector) is  $\mathbf{w} = (r, a, b)$ , for example: (6, 2, 3).

We assume that the *a* and *b* are input values.

Distributed Lab zk-SNARK I 16 / 28 Sep 5, 2024 16 / 28

### Example

```
def multiply (a: F, b: F) \rightarrow F:
     return a * b
```

This can be represented as a circuit with only one (multiplication) gate:

$$r = a \times b$$

The witness vector (essentially, our solution vector) is  $\mathbf{w} = (r, a, b)$ , for example: (6, 2, 3).

We assume that the a and b are input values.

#### Note

We can think of the "=" in the gate as an assertion.

16 / 28

### Example

Now, suppose we want to implement the evaluation of the polynomial  $Q(x_1, x_2) = x_1^3 + x_2^2 \in \mathbb{F}[x_1, x_2]$  using arithmetic circuits.

Looks easy, right? But the circuit is now much less trivial.

$$x_1^2 = x_1 \times x_1$$
  $r_1 = x_1 \times x_1$   
 $x_1^3 = x_1^2 \times x_1$  or  $r_2 = r_1 \times x_1$   
 $x_2^2 = x_2 \times x_2$  or  $r_3 = x_2 \times x_2$   
 $Q = x_1^3 + x_2^2$   $Q = r_2 + r_3$ 

Distributed Lab zk-SNARK I 17 / 28 Sep 5, 2024 17 / 28

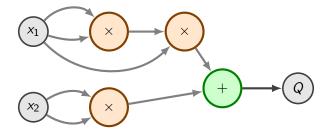


Figure: Example of a circuit evaluating  $x_1^3 + x_2^2$ .

Distributed Lab zk-SNARK I 18 / 28 Sep 5, 2024 18 / 28

### Example

Well, it is quite clear how to represent any polynomial-like expressions. But how can we translate if statements?

```
def example(a: bool, b: F, c: F) -> F:
    if a:
        return b * c
    else:
        return b + c
```

### Example

Well, it is quite clear how to represent any polynomial-like expressions. But how can we translate if statements?

```
def example(a: bool, b: F, c: F) -> F:
    if a:
        return b * c
    else:
        return b + c
```

We can transform such a function into the next expression:

$$r = a \times (b \times c) + (1 - a) \times (b + c)$$

Distributed Lab zk-SNARK I 19 / 28 Sep 5, 2024 19 / 28

### Example

Well, it is quite clear how to represent any polynomial-like expressions. But how can we translate if statements?

```
def example(a: bool, b: F, c: F) -> F:
    if a:
        return b * c
    else:
        return b + c
```

We can transform such a function into the next expression:

$$r = a \times (b \times c) + (1 - a) \times (b + c)$$

Corresponding equations for the circuit are:

$$r_1 = b \times c,$$
  $r_3 = 1 - a,$   $r_5 = r_3 \times r_2$   
 $r_2 = b + c,$   $r_4 = a \times r_1,$   $r = r_4 + r_5$ 

Distributed Lab zk-SNARK I 19 / 28 Sep 5, 2024 19 / 28

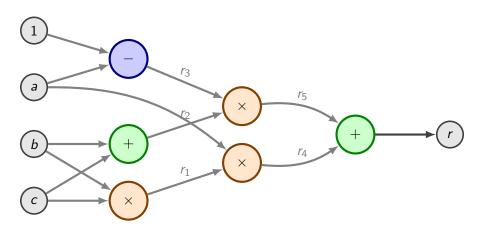


Figure: Example of a circuit evaluating the if statement logic.

Distributed Lab zk-SNARK I 20 / 28 Sep 5, 2024 20 / 28

# Circuit Satisfability Problem

#### **Definition**

Arithmetic circuit  $C: \mathbb{F}^N \to \mathbb{F}$  over a finite field  $\mathbb{F}$  is a directed acyclic graph where internal nodes are labeled via +, -, and  $\times$ , and inputs are labeled  $1, x_1, x_2, \ldots, x_n$ . By |C| we denote the number of gates in the circuit.

# Circuit Satisfability Problem

#### Definition

Arithmetic circuit  $C: \mathbb{F}^N \to \mathbb{F}$  over a finite field  $\mathbb{F}$  is a directed acyclic graph where internal nodes are labeled via +, -, and  $\times$ , and inputs are labeled  $1, x_1, x_2, \ldots, x_n$ . By |C| we denote the number of gates in the circuit.

#### Definition

The **Circuit Satisfiability Problem** is defined as follows: given an arithmetic circuit C and a public input  $x \in \mathbb{F}^n$ , determine if there exists a private input  $w \in \mathbb{F}^m$  such that C(x,w)=0. More formally, the problem is determined by relation  $\mathcal{R}_{\mathbb{C}}$  and corresponding language  $\mathcal{L}_{\mathbb{C}}$  as follows:

$$\mathcal{R}_{C} = \{(x, w) \in \mathbb{F}^{n} \times \mathbb{F}^{m} \mid C(x, w) = 0\},\$$
  
$$\mathcal{L}_{C} = \{x \in \mathbb{F}^{n} \mid \exists w \in \mathbb{F}^{m} : C(x, w) = 0\}$$

Distributed Lab zk-SNARK I 21 / 28 Sep 5, 2024 21 / 28

# Rank-1 Constraint System

Distributed Lab zk-SNARK I 22 / 28 Sep 5, 2024 22

### Inner Product

#### **Definition**

The **inner product** of a linear space V is any symmetric, linear in the first argument, and positive binary function from vector space to a set of scalars.

$$\langle \cdot, \cdot \rangle : \mathbb{V} \times \mathbb{V} \to \mathbb{F}$$

 $\forall \mathbf{u}, \mathbf{v}, \mathbf{w} \in \mathbb{V}, \forall a \in \mathbb{F}$  the following properties are satisfied:

- Symmetry:  $\langle \mathbf{u}, \mathbf{v} \rangle = \langle \mathbf{v}, \mathbf{u} \rangle$
- Linearity in the first argument:  $\langle c\mathbf{u} + \mathbf{v}, \mathbf{w} \rangle = c \langle \mathbf{u}, \mathbf{w} \rangle + \langle \mathbf{v}, \mathbf{w} \rangle$
- Positivity:  $\langle \mathbf{u}, \mathbf{u} \rangle \ge 0$  and  $\langle \mathbf{u}, \mathbf{u} \rangle = 0 \Leftrightarrow \mathbf{u} = 0$

Plenty of functions can be built that satisfy the inner product definition, we'll use the one that is usually called **dot product**.

### Dot Product

#### **Definition**

Let  $\mathbb V$  be a vector space over the field  $\mathbb F$ . The **dot product** on  $\mathbb V$  is a function:

$$\langle \cdot, \cdot \rangle : \mathbb{V} \times \mathbb{V} \to \mathbb{F}$$

defined for  $\mathbf{u}, \mathbf{v} \in \mathbb{V}$  as follows:

$$\langle \mathbf{u}, \mathbf{v} \rangle = \sum_{i=1}^n u_i v_i$$



Distributed Lab zk-SNARK I 24 / 28 Sep 5, 2024 24 / 28

### Dot Product

#### Definition

Let  $\mathbb V$  be a vector space over the field  $\mathbb F$ . The **dot product** on  $\mathbb V$  is a function:

$$\langle \cdot, \cdot \rangle : \mathbb{V} \times \mathbb{V} \to \mathbb{F}$$

defined for  $\mathbf{u}, \mathbf{v} \in \mathbb{V}$  as follows:

$$\langle \mathbf{u}, \mathbf{v} \rangle = \sum_{i=1}^n u_i v_i$$

#### Note

The dot product can also be denoted using the dot notation as:

$$\mathbf{u}\cdot\mathbf{v}$$

That is why it's called the "dot" product.

Sep 5, 2024

### **Dot Product**

### Example

Let  $\mathbf{u}, \mathbf{v}$  are vectors over the real number  $\mathbb{R}$ , where

$$\mathbf{u} = (1, 2, 3), \quad \mathbf{v} = (2, 4, 3)$$

Then:

$$\langle \mathbf{u}, \mathbf{v} \rangle = \sum_{i=1}^{3} u_i v_i = 2 \cdot 1 + 2 \cdot 4 + 3 \cdot 3 = 2 + 8 + 9 = 19$$

Distributed Lab zk-SNARK I 25 / 28 Sep 5, 2024 25 / 28

## Rank-1 Constraint System

With knowledge of the dot product of two vectors, we can now formulate a definition of the constraint in the context of the R1CS.

#### **Definition**

Each **constraint** in the Rank-1 Constraint System must be in the form:

$$\langle \mathsf{a}, \mathsf{w} \rangle \times \langle \mathsf{b}, \mathsf{w} \rangle = \langle \mathsf{c}, \mathsf{w} \rangle$$

Where  $\mathbf{w}$  is a vector containing all the *input*, *output*, and *intermediate* variables involved in the computation. The vectors  $\mathbf{a}$ ,  $\mathbf{b}$ , and  $\mathbf{c}$  are vectors of coefficients corresponding to these variables, and they define the relationship between the linear combinations of  $\mathbf{w}$  on the left-hand side and the right-hand side of the equation.

Distributed Lab zk-SNARK I 26 / 28 Sep 5, 2024 26 / 28

### Rationale Behind The Structure Of R1CS

Distributed Lab zk-SNARK I 27 / 28 Sep 5, 2024 27 / 28

# Quadratic Arithmetic Program

Distributed Lab zk-SNARK I 28 / 28 Sep 5, 2024 28 / 28